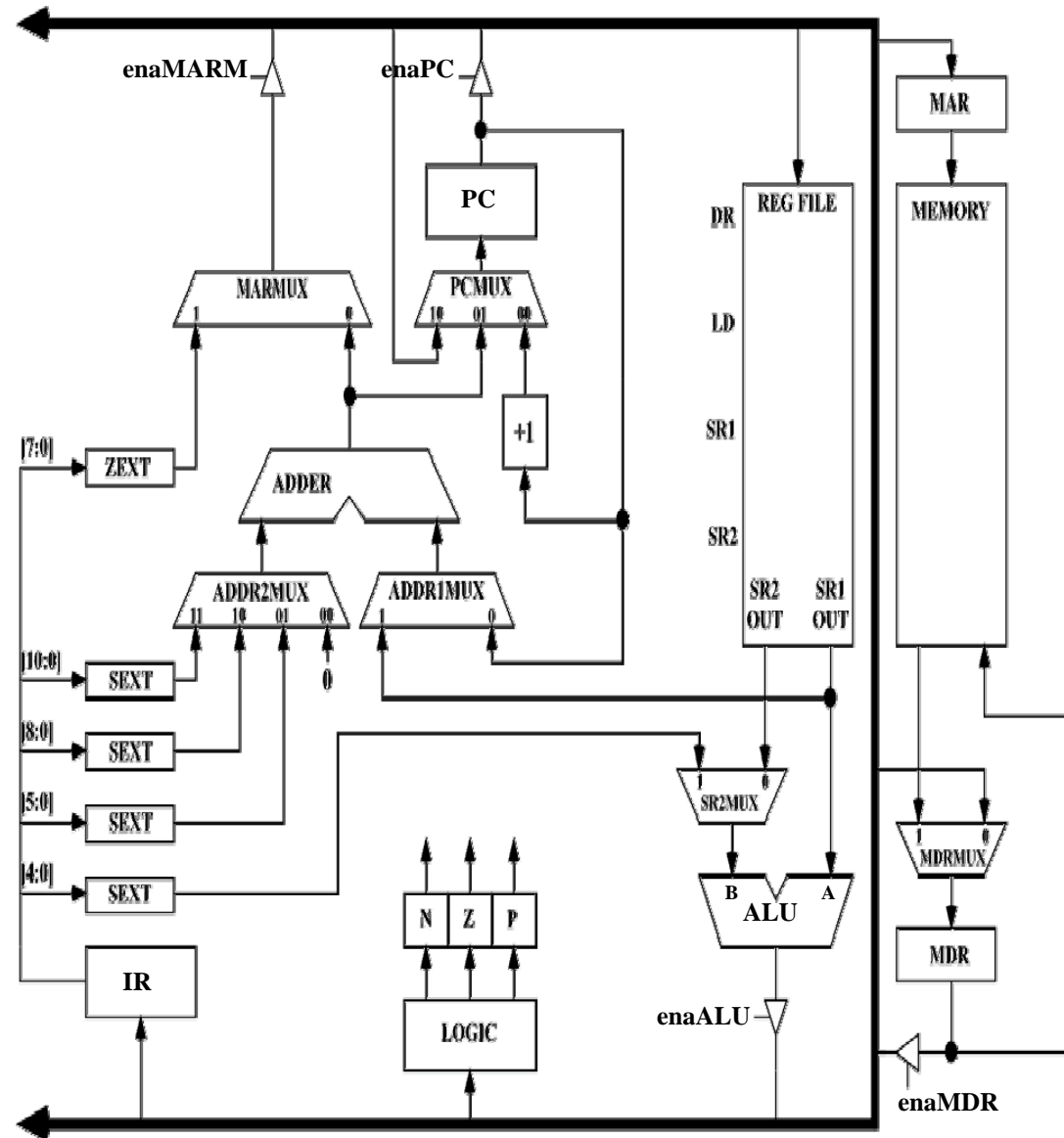


# LC3-2

## The LC-3 Datapath




# Datapath Strategy


- ◆ Take datapath elements one-by-one
- ◆ Determine how each works
- ◆ Clearly identify inputs/outputs and needed control
- ◆ Design the element
- ◆ When all done, doing control is straightforward...
  - Push all the complexity into the datapath that we can
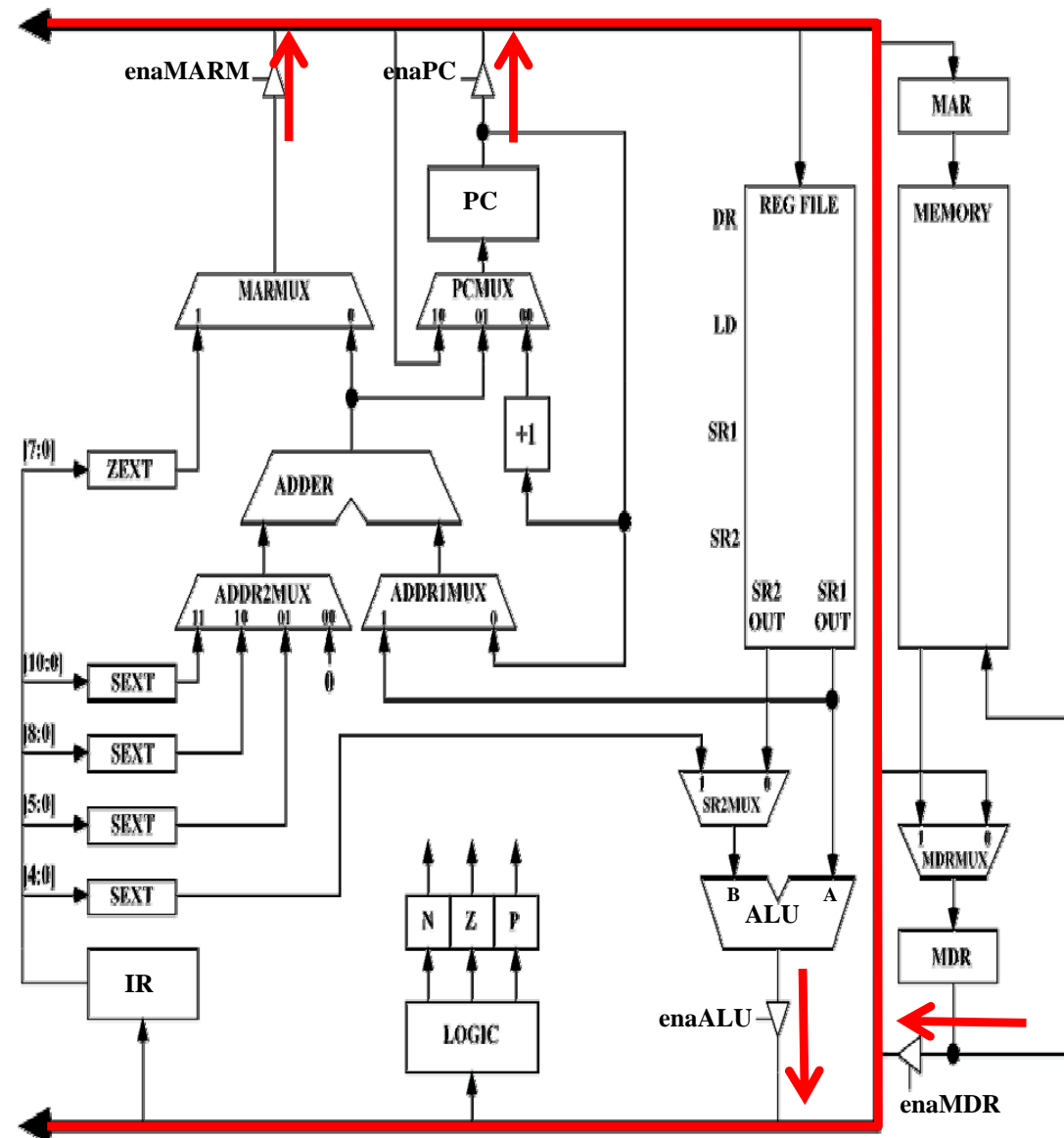
# The Bus



- ◆ Four major drivers: MARMUX, PC, ALU, MDR
- ◆ It is the means of data transfer between units.



# Tri-State Drivers

 
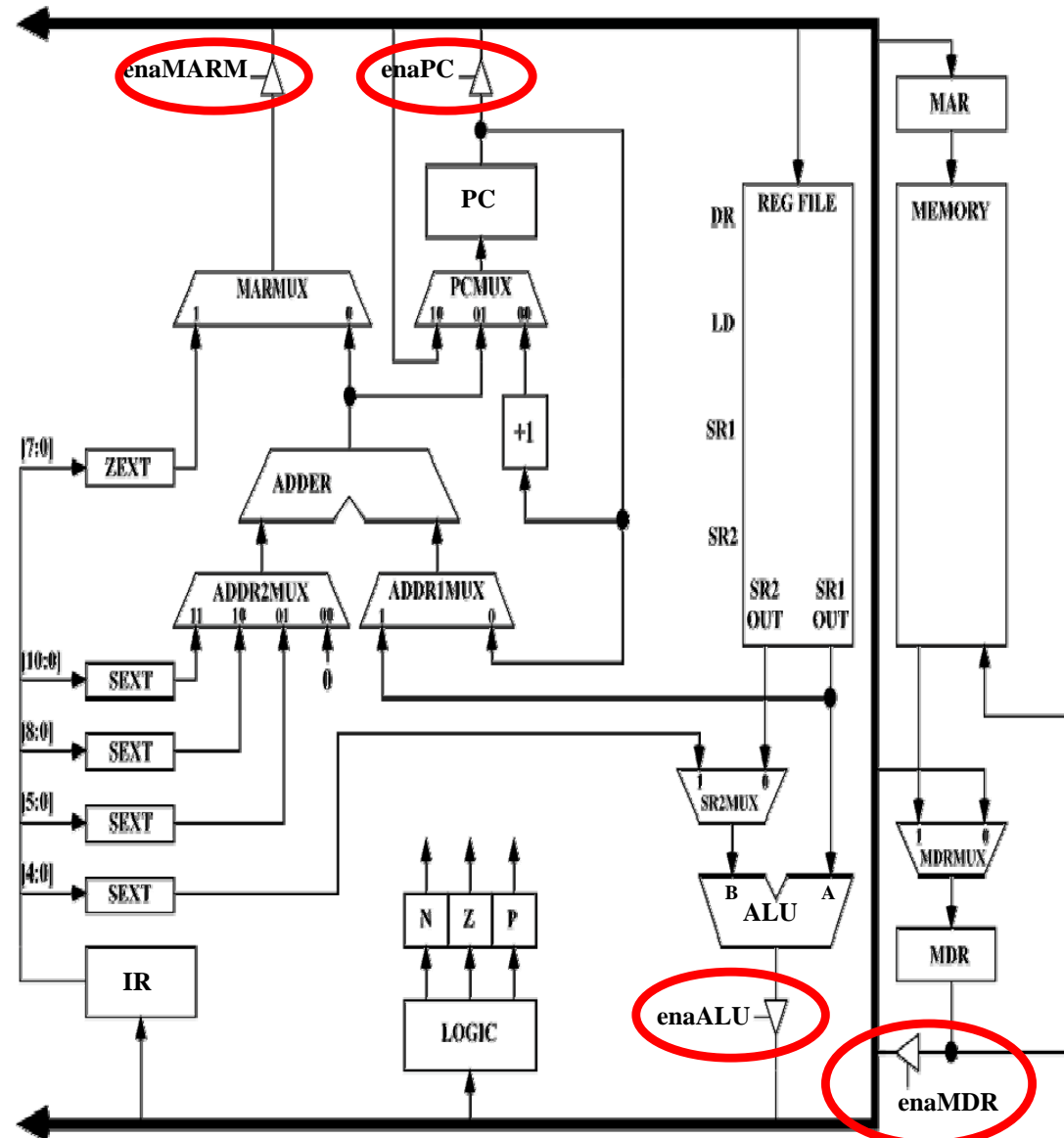 
```
module ts_driver ( din, dout, en );
  input [15:0] din;
  output [15:0] dout;
  input en;
  assign dout = en ? din : 16'hZZZZ;
endmodule
```




# More Tri-State

## ◆ Lots of drivers and lots of listeners

- *Only one driver on at any time*
- It's a distributed MUX!

 
**Be careful!**

If more than one driver is on at once there will be contention on the bus with unpredictable results




# Typical Tri-State Drivers

en	din	dout
0	0	Z
0	1	Z
1	0	0
1	1	1

 

t	din	dout
0	0	0
0	1	1
1	0	Z
1	1	Z

 

- ◆ An adder, two muxes, and three sign extenders

```



IR[10:0]
Ra[15:0]
PC[15:0]
selEAB1
selEAB2[1:0]
eabOut[15:0]

```



  
# The Effective Address Block

Why are there 3 different sign extenders?





# Designing the EAB

 

- ◆ Simply a MUX and a zero extender


- IR[7:0]

# seIMAR

MARMUXOut[15:0]



# Designing the MARMUX

 

- ◆ A register, MUX, and an incrementer

clk


selPC[1:0]

# IdPC

Buss[15:0]



# Designing the PC

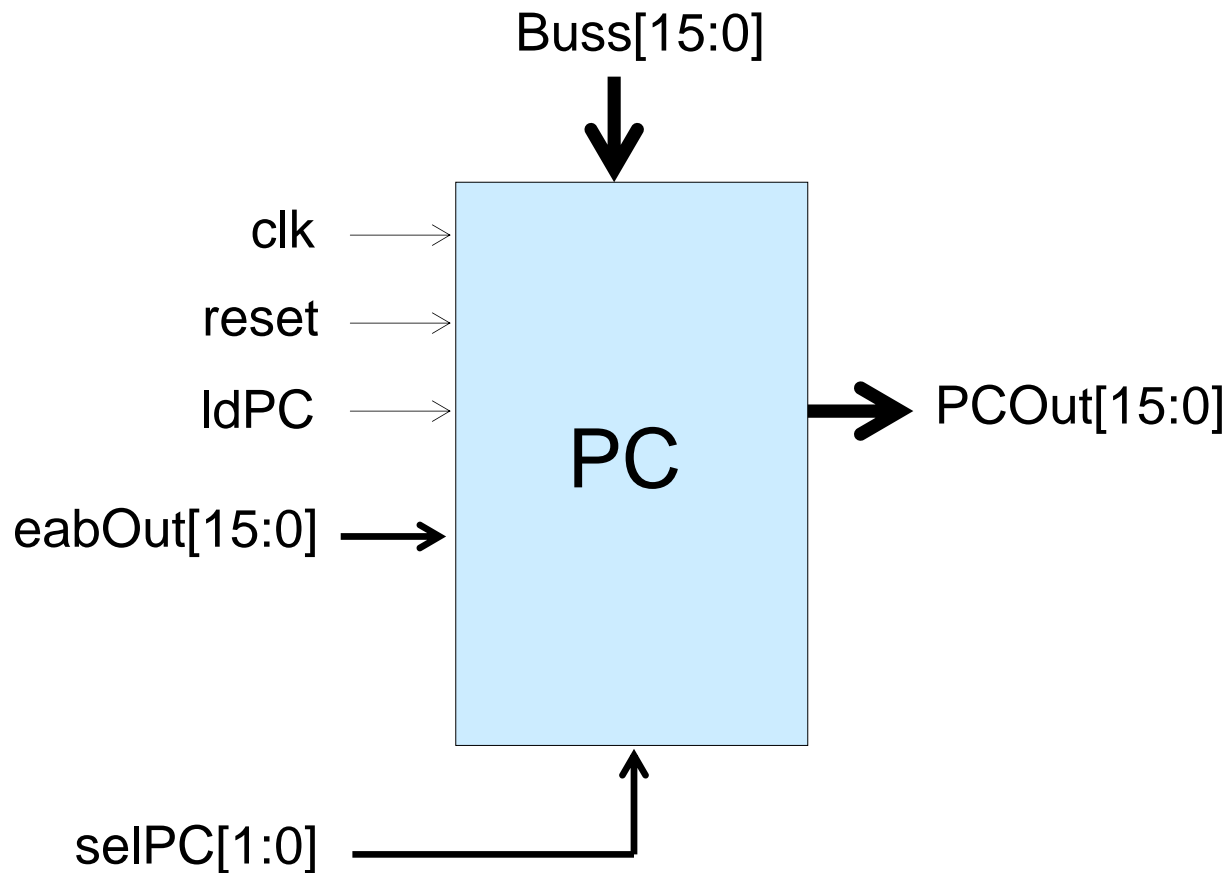

**NOTE: Be sure your PC initializes to 0 on a global reset**

# The IR

- Simply a loadable register, loads from bus when enabled for loading

- Signals:


clk

reset


ldIR

Buss[15:0]

IR[15:0]

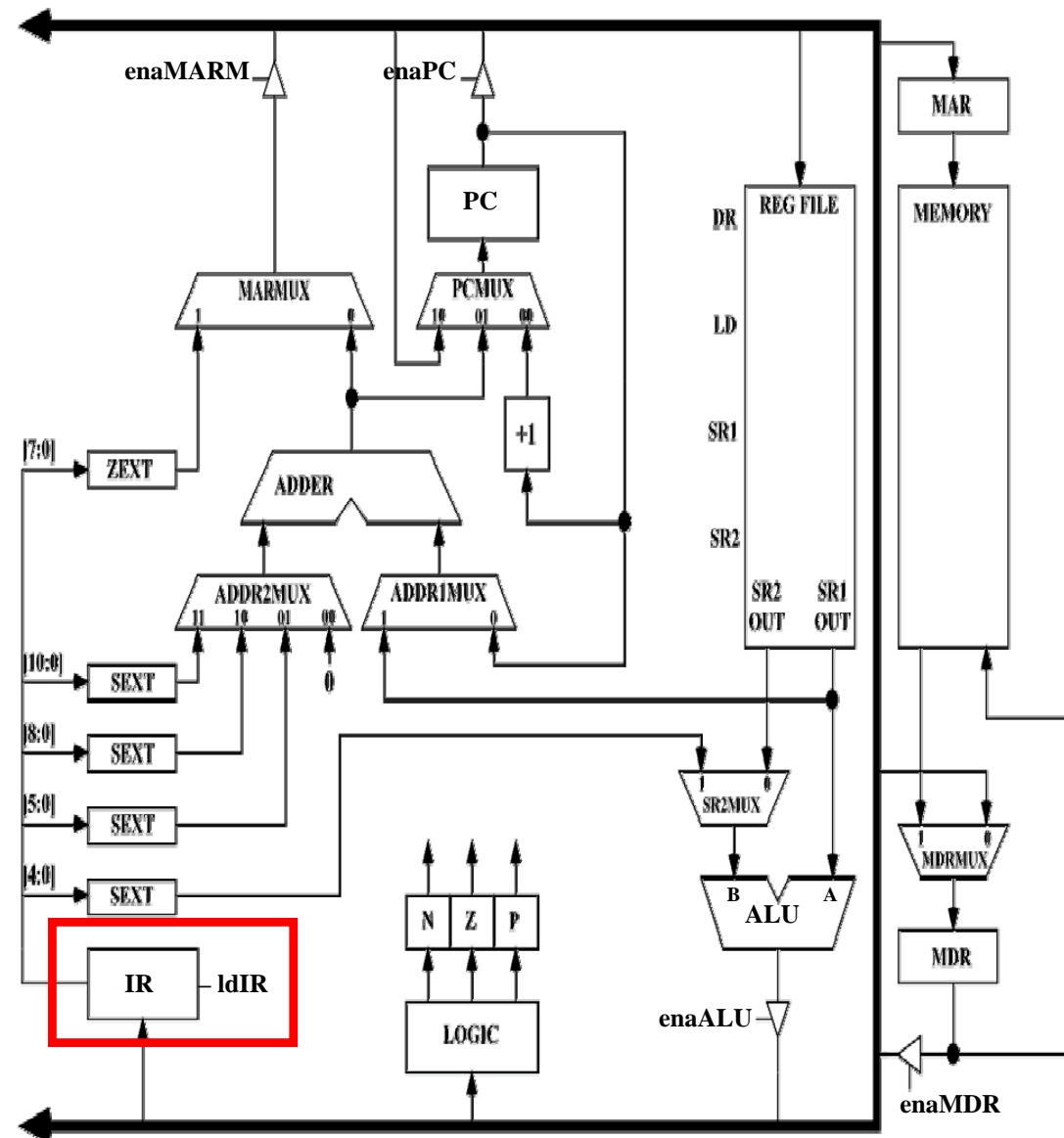


# Designing the IR

 
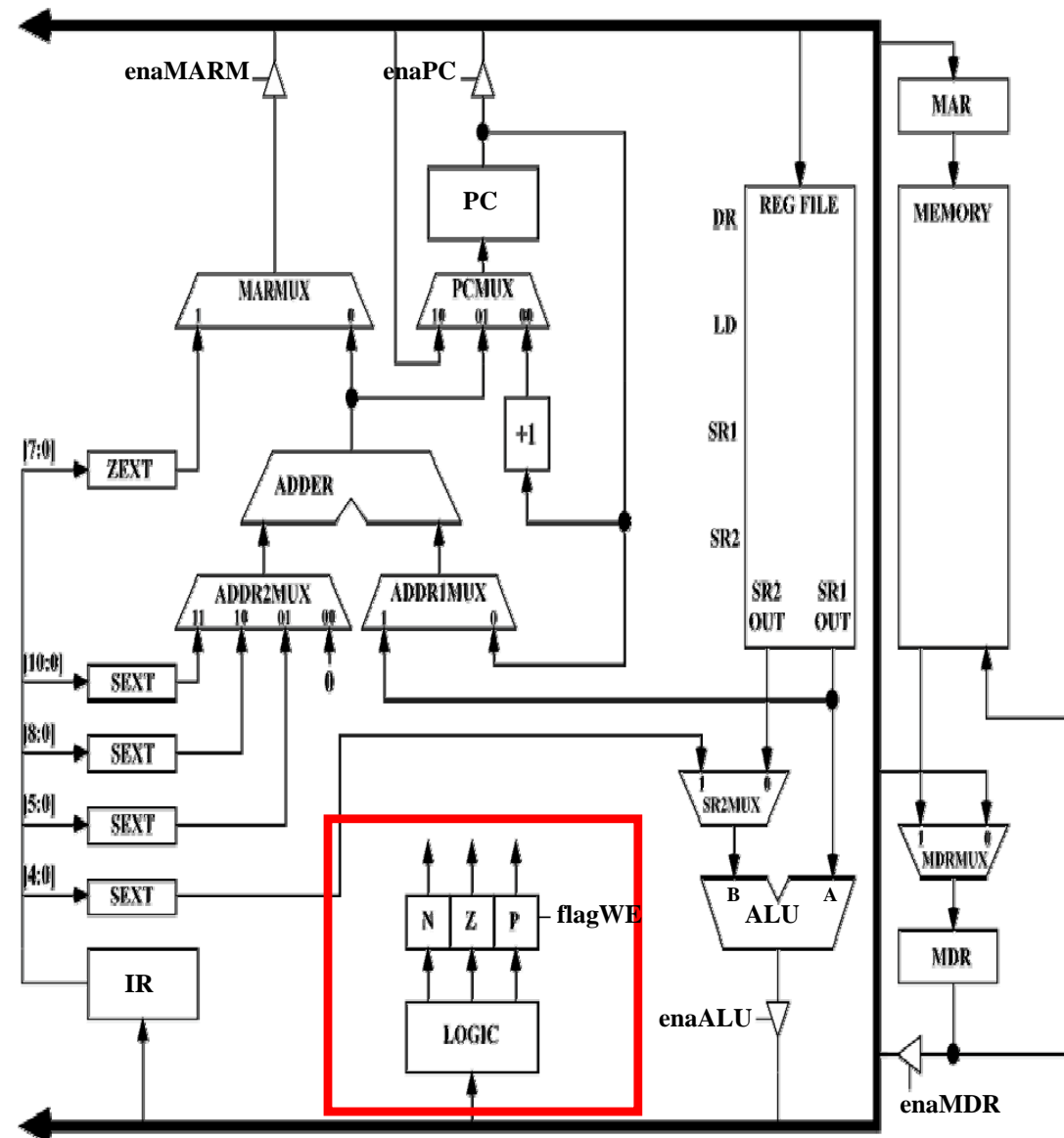
# The nzp Flags


- ◆ Loadable registers which contain flags.
- ◆ Load on *some* reg writes
- ◆ Decode bus to determine flag values
- ◆ Signals:

clk  
reset  
flagWE  
Buss[15:0]  
N  
Z  
P






# Designing the nzp Flags

 


**How many of N, Z, P can be high at one time?**

- ◆ Has 4 functions:  
add, and, not, pass
- ◆ One operand always comes from regfile, other from mux
- ◆ Signals:


aluOut[15:0]

 


# The Operate Instructions

 


DR = SR1 + SR2

 


DR = SR1 + SIGNEXTEND(imm5)

 

DR = SR1 AND SR2

 


DR = SR1 AND SIGNEXTEND(imm5)

 

DR = NOT(SR1)


# Designing the ALU

 


# The Memory

- ◆ Writes on clock edge when **memWE=1**
- ◆ Data read from and written to memory passes through MDR
- ◆ The MDRMUX controls where data is loaded from
- ◆ Signals:

clk	reset
selMDR	ldMAR
memWE	ldMDR
Buss[15:0]	mdrOut[15:0]

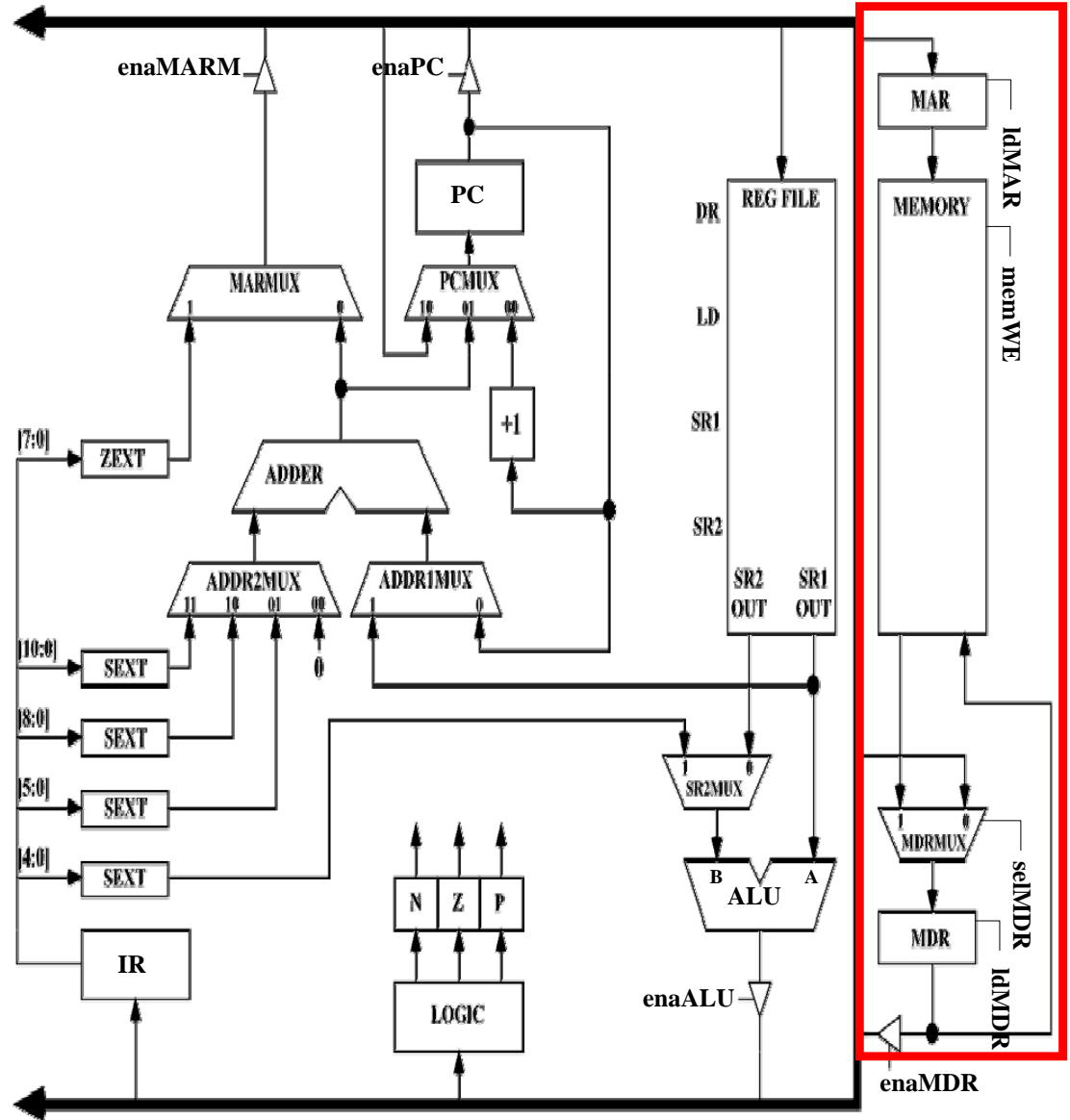

# Designing the Memory

 

- ◆ Triple-ported memory (2 read ports, 1 write port)
- ◆ Synchronous write, asynchronous read
- ◆ Signals:

**BYU**  
Computer Engineering  
Electrical Engineering



# Register File Signals

- ◆ DR is either “111” (subroutine call) or comes from IR[11:9]
- ◆ SR2 is always IR[2:0]
- ◆ SR1 changes depending on the instruction
  - IR[11:9] on STI, ST
  - IR[11:9] in one state associated with STR
  - “111” on RET (same as IR[8:6])
  - IR[8:6] otherwise
- ◆ regWE is generated by the control block




# LC-3 Instructions


ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCoffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCoffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	

LD	0010	DR	PCoffset9										
LDI	1010	DR	PCoffset9										
LDR	0110	DR	BaseR	offset6									
LEA	1110	DR	PCoffset9										
ST	0011	SR	PCoffset9										
STI	1011	SR	PCoffset9										
STR	0111	SR	BaseR	offset6									
TRAP	1111	0000	trapvect8										
RTI	1000	000000000000											
reserved	1101												

# Building the Register File

 


# Building the Register File

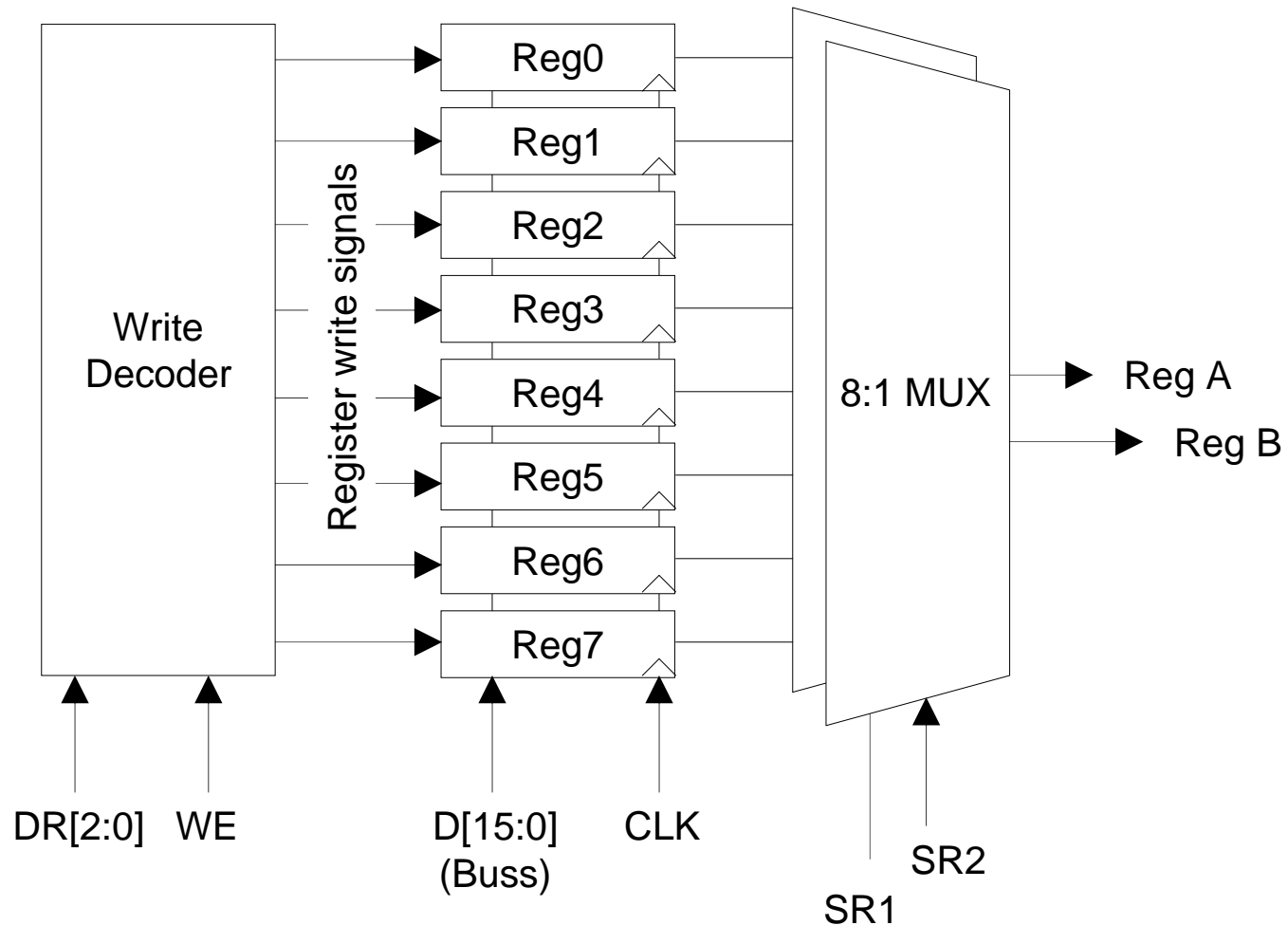

# Building the Machine

- ◆ Each element of the datapath can be considered independently, designed independently, and debugged independently
- ◆ Once this has been done the control can be easily completed

# The LC-3

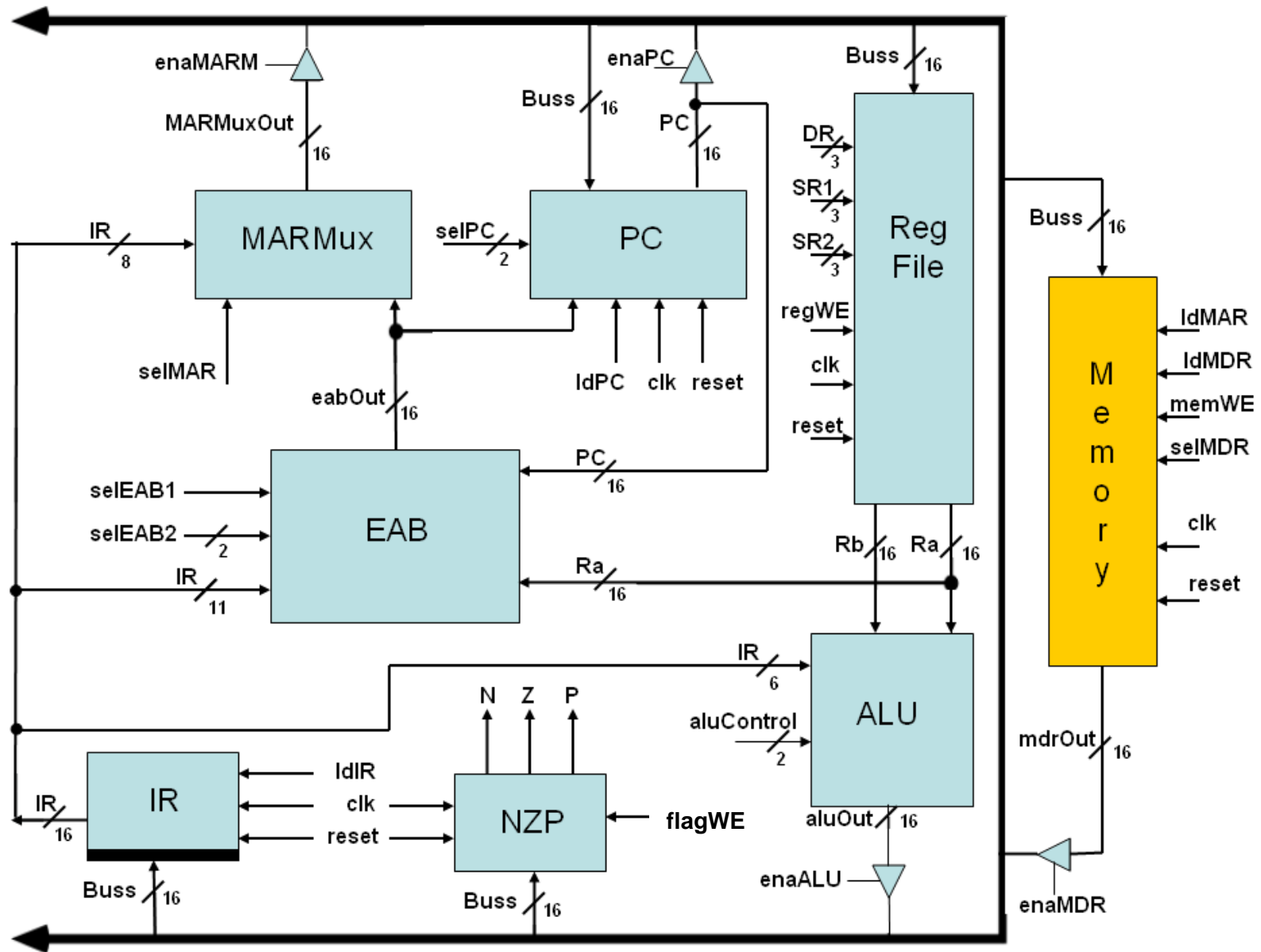

# The LC-3

